

## ***Design Calculations for Buck-Boost Converters***

Michael Green

Advanced Low Power Solutions

### **ABSTRACT**

This application note gives the equations to calculate the power stage of a non-inverting buck-boost converter built with an IC with integrated switches and operating in continuous conduction mode. See the references at the end of this document if more detail is needed.

For a design example without description, see appendix A.

### **Contents**

<b>1</b>	<b>Basic Configuration of a Buck Boost Converter .....</b>	<b>2</b>
1.1	Necessary Parameters of the Power Stage .....	2
<b>2</b>	<b>Calculating the Duty Cycle .....</b>	<b>2</b>
<b>3</b>	<b>Inductor Selection .....</b>	<b>3</b>
3.1	Buck Mode .....	3
3.2	Boost Mode .....	3
<b>4</b>	<b>Calculating Maximum Switch Current.....</b>	<b>4</b>
4.1	Buck Mode .....	4
4.2	Boost Mode .....	5
<b>5</b>	<b>Output Voltage Setting.....</b>	<b>5</b>
<b>6</b>	<b>Input Capacitor Selection .....</b>	<b>7</b>
<b>7</b>	<b>Output Capacitor Selection .....</b>	<b>7</b>
7.1	Buck Mode .....	7
7.2	Boost Mode .....	8
	<b>References.....</b>	<b>9</b>
	<b>Appendix A. Design Example Using TPS63020 .....</b>	<b>10</b>
A.1	System Requirements .....	10
A.2	Duty Cycle .....	10
A.3	Inductor Selection .....	10
A.4	Maximum Switch Current.....	10
A.5	Output Voltage Setting.....	10
A.6	Input Capacitor Selection.....	10
A.7	Output Capacitor Selection.....	11

### **Figures**

<b>Figure 1.</b>	<b>Buck Boost Converter Schematic .....</b>	<b>2</b>
<b>Figure 2.</b>	<b>Feedback Circuit.....</b>	<b>6</b>

## 1 Basic Configuration of a Buck Boost Converter

Figure 1, shows the basic configuration of a buck-boost converter where the switches are integrated in the IC. Many of the Advanced Low Power buck-boost converters (TPS63xxx) have all four switches integrated in the IC. This reduces solution size and eases the difficulty of the design.

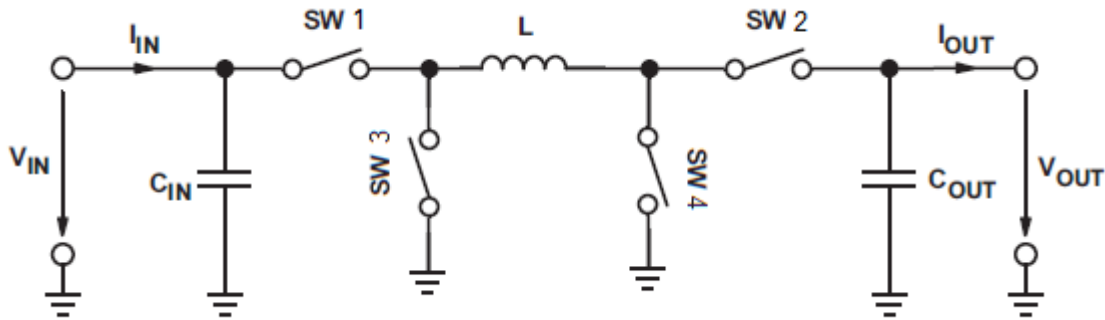


Figure 1. Buck Boost Converter Schematic

### 1.1 Necessary Parameters of the Power Stage

The following four parameters are needed to calculate the power stage:

1. Input voltage range:  $V_{inmin}$  and  $V_{inmax}$
2. Nominal output voltage:  $V_{out}$
3. Maximum output current:  $I_{out}$
4. Integrated circuit used to build the buck-boost converter. This is necessary because some parameters for the calculations must be derived from the data sheet.

If these parameters are known, the power stage can be calculated.

## 2 Calculating the Duty Cycle

The first step after selecting the operating parameters of the converter is to calculate the minimum duty cycle for buck mode and maximum duty cycle for boost mode. These duty cycles are important because at these duty cycles the converter is operating at the extremes of its operating range. The duty cycle is always positive and less than 1.

$$D_{buck} = \frac{V_{out} \times \eta}{V_{inmax}} \quad (1)$$

$$D_{boost} = 1 - \frac{V_{inmin} \times \eta}{V_{out}} \quad (2)$$

Where:

$V_{inmax}$  = maximum input voltage  
 $V_{inmin}$  = minimum input voltage  
 $V_{out}$  = desired output voltage  
 $D_{buck}$  = minimum duty cycle for buck mode  
 $D_{boost}$  = maximum duty cycle for boost mode  
 $\eta$  = estimated efficiency at calculated  $V_{in}$ ,  $V_{out}$ , and  $I_{out}$

### 3 Inductor Selection

Data sheets often give a range of recommended inductor values. If this is the case, choose an inductor from this range. The higher the inductor value, the higher is the possible maximum output current because of the reduced ripple current.

Normally, the lower the inductor value, the smaller is the solution size. Note that the inductor must always have a higher current rating than the largest value of current given from Equations 5 and 8; this is because the peak current increases with decreasing inductance.

For device datasheets, where no inductor range is given, an inductor that satisfies both buck and boost mode conditions must be chosen. Follow both sections 3.1 and 3.2 to find the right inductance. Select the largest value of inductance calculated from either equations 3 and 4.

#### 3.1 Buck Mode

For buck mode the following equation is a good estimate for the right inductance:

$$L > \frac{V_{out} \times (V_{inmax} - V_{out})}{K_{ind} \times F_{sw} \times V_{inmax} \times I_{out}} \quad (3)$$

Where:

$V_{inmax}$  = maximum input voltage

$V_{out}$  = desired output voltage

$I_{out}$  = desired maximum output current

$F_{sw}$  = switching frequency of the converter

$K_{ind}$  = estimated coefficient that represents the amount of inductor ripple current relative to the maximum output current.

A good estimation for the inductor ripple current is 20% to 40% of the output current, or  $0.2 < K_{ind} < 0.4$ .

#### 3.2 Boost Mode

For boost mode the following equation is a good estimate for the right inductance:

$$L > \frac{V_{inmin}^2 \times (V_{out} - V_{inmin})}{F_{sw} \times K_{ind} \times I_{out} \times V_{out}^2} \quad (4)$$

Where:

$V_{inmin}$  = minimum input voltage

$V_{out}$  = desired output voltage

$I_{out}$  = desired maximum output current  
 $F_{sw}$  = switching frequency of the converter  
 $K_{ind}$  = estimated coefficient that represents the amount of inductor ripple current relative to the maximum output current.

A good estimation for the inductor ripple current is 20% to 40% of the output current, or  $0.2 < K_{ind} < 0.4$ .

## 4 Calculating Maximum Switch Current

To calculate the maximum switch current the duty cycle must be derived as done in section 2 of this application note. There are two operating cases to consider for these calculations: buck and boost mode. Derive the maximum switch current for both cases. Use the greater of the two switch currents for remainder of this application note.

### 4.1 Buck Mode

In buck mode, the maximum switch current is when the input voltage is at its maximum. Using equations 5 and 6, the maximum switch current can be calculated.

$$I_{swmax} = \frac{\Delta I_{max}}{2} + I_{out} \quad (5)$$

$$\Delta I_{max} = \frac{(V_{inmax} - V_{out}) \times D_{buck}}{F_{sw} \times L} \quad (6)$$

Where:

$V_{inmax}$  = maximum input voltage

$V_{out}$  = desired output voltage

$I_{out}$  = desired output current

$\Delta I_{max}$  = maximum ripple current through the inductor

$I_{swmax}$  = maximum switch current

$D_{buck}$  = minimum duty cycle for buck mode

$F_{sw}$  = switching frequency of the converter

$L$  = selected inductor value

To obtain the switching frequency, refer to the datasheet for the given converter.

Before continuing, verify that the converter can deliver the maximum current using equation 7.  $I_{maxout}$  must be greater than  $I_{out}$ .

$$I_{maxout} = I_{lim} - \frac{\Delta I_{max}}{2} \quad (7)$$

Where:

$I_{maxout}$  = maximum deliverable current through inductor by the converter

$I_{lim}$  = switch current limit, specified in converter datasheet

$\Delta I_{max}$  = Ripple current through the inductor calculated in equation 6.

## 4.2 Boost Mode

In boost mode, the maximum switch current is when the input voltage is at its minimum. Using equations 8 and 9, the maximum switch current can be calculated.

$$I_{swmax} = \frac{\Delta I_{max}}{2} + \frac{I_{out}}{1-D_{boost}} \quad (8)$$

$$\Delta I_{max} = \frac{V_{inmin} \times D_{boost}}{F_{sw} \times L} \quad (9)$$

Where:

$V_{inmin}$  = minimum input voltage

$V_{out}$  = desired output voltage

$I_{out}$  = desired output current

$\Delta I_{max}$  = maximum ripple current through the inductor

$I_{swmax}$  = maximum switch current

$D_{boost}$  = maximum duty cycle for boost mode

$F_{sw}$  = switching frequency of the converter

$L$  = selected inductor value

To obtain the switching frequency, refer to the datasheet for the given converter.

Before continuing, verify that the converter can deliver the maximum current using equation 10.  $I_{maxout}$  must be greater than  $I_{outmax}$ .  $I_{outmax}$  is specified as the maximum output current required by the application.

$$I_{maxout} = \left( I_{lim} - \frac{\Delta I_{max}}{2} \right) \times (1 - D_{boost}) \quad (10)$$

Where:

$I_{maxout}$  = maximum deliverable current through inductor by the converter

$D_{boost}$  = maximum duty cycle for boost mode


$I_{lim}$  = switch current limit, specified in converter datasheet

$\Delta I_{max}$  = Ripple current through the inductor calculated in equation 9.

## 5 Output Voltage Setting

Most converters set the output voltage with a resistive divider network. This is integrated if the converter is a fixed output voltage converter. In this case, the external voltage divider described in this section is not used.

With the given feedback voltage,  $V_{FB}$ , and feedback bias current,  $I_{FB}$ , the voltage divider can be calculated.

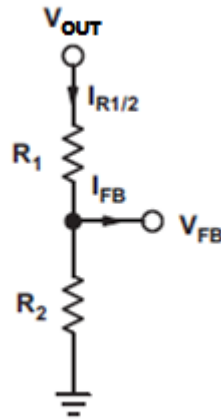

**Figure 2. Feedback Circuit**

The current through the resistive divider must be at least 100 times the size of the feedback bias current. SLYT469 is also available for a detailed discussion on resistive feedback divider design.

$$I_{R1/2} \geq 100 \times I_{FB} \quad (11)$$

Where:

$I_{R1/2}$  = current through the resistive divider to GND

$I_{FB}$  = feedback bias current from data sheet

This adds less than 1% inaccuracy to the voltage measurement. For the calculation of the feedback divider, the current into the feedback pin can be neglected. The disadvantage of using smaller resistor values than computed from equations 12 and 13 is a higher power loss in the resistive divider and thus lower efficiency at light loads, but the accuracy does increase. Again, for a more detailed discussion on this subject matter see the SLYT469.

Neglecting the current into the FB pin, the resistors are calculated as followed:

$$R2 = \frac{V_{fb}}{\frac{I_{R1}}{2}} \quad (12)$$

$$R1 = R2 \times \left( \frac{V_{out}}{V_{fb}} - 1 \right) \quad (13)$$

Where:

$R_1, R_2$  = resistive divider values, see Figure 2.

$V_{fb}$  = feedback voltage from the datasheet

$I_{R1/2}$  = current through the resistive divider to GND, calculated in Equation 11

$V_{OUT}$  = desired output voltage

## 6 Input Capacitor Selection

The minimum value for the input capacitor is normally given in the datasheet. This minimum value is necessary to stabilize the input voltage due to the peak current requirement of a switching power supply. The best practice is to use low-equivalent series resistance (ESR) ceramic capacitors. The dielectric material must be X5R or better. Otherwise, the capacitor loses much of its capacitance due to dc bias or temperature.

The value can be increased if the input voltage is noisy.

## 7 Output Capacitor Selection

The best practice is to use low-ESR capacitors to minimize the ripple on the output voltage. Ceramic capacitors are a good choice if the dielectric material is X5R or better.

If the converter has external compensation, any capacitor value above the recommended minimum in the datasheet can be used, but the compensation has to be adjusted for the used output capacitance.

With internally compensated converters, the recommended inductor and capacitor values must be used, or the recommendations in the datasheet for adjusting the output capacitors to the application must be followed. This usually involves keeping the same ratio of  $L \times C$  as the recommended values.

With external compensation, a solution that satisfies both buck and boost mode must be chosen. Follow both sections 7.1 and 7.2 to develop minimum output capacitance for both buck and boost mode operations. Select output capacitance that is larger than both minimum required output capacitance for buck and boost mode operation. Always account for DC bias capacitance drop and derate the capacitance of the output capacitors for the design calculations.

### 7.1 Buck Mode

For buck mode, equations 14 and 16 are used to calculate the minimum output capacitor value for a desired output voltage ripple. For the minimum output capacitance use the maximum value from equation 14 and 16.

$$C_{outmin1} = \frac{K_{ind} \times I_{out}}{8 \times F_{sw} \times V_{out_{ripple}}} \quad (14)$$

Where:

$C_{outmin1}$  = minimum output capacitance required

$F_{sw}$  = switching frequency of the converter

$V_{out_{ripple}}$  = desired output voltage ripple

$I_{out}$  = desired maximum output current

$K_{ind}$  = estimated coefficient that represents the amount of inductor ripple current relative to the maximum output current.

The ESR of the output capacitor adds some more ripple, which can be calculated with equation 15:

$$\Delta V_{out_{esr}} = ESR \times K_{ind} \times I_{out} \quad (15)$$

Where:

$\Delta V_{out_{esr}}$  = additional output voltage ripple due to capacitors ESR

ESR = equivalent series resistance of the used output capacitor

Often the selection of the output capacitor is not driven by the steady-state ripple, but by the output transient response. The output voltage deviation is caused by the time it takes the inductor to catch up with the increased or reduced output current needs.

The following formula can be used to calculate the necessary output capacitance for a desired maximum overshoot caused by the removal of the load current.

$$C_{outmin2} = \frac{(K_{ind} \times I_{out})^2 \times L}{2 \times V_{out} \times \Delta V_{out}} \quad (16)$$

Where:

$C_{outmin2}$  = minimum output capacitance required for a desired overshoot

$I_{out}$  = desired maximum output current

$K_{ind}$  = estimated coefficient that represents the amount of inductor ripple current relative to the maximum output current

$V_{out}$  = desired output voltage

$\Delta V_{out}$  = desired output voltage change due to the overshoot

## 7.2 Boost Mode

With external compensation, the following equations can be used to adjust the output capacitor values for a desired output voltage ripple:

$$C_{outmin} = \frac{I_{out} \times D_{boost}}{F_{sw} \times \Delta V_{out}} \quad (17)$$

Where:

$C_{outmin}$  = minimum output capacitance

$I_{OUT}$  = maximum output current of the application

$D_{boost}$  = duty cycle calculated with Equation 7

$F_{sw}$  = switching frequency of the converter

$\Delta V_{out}$  = desired output voltage ripple

The ESR of the output capacitor adds some more ripple, given with the equation 18. Be sure to account for this  $V_{out}$  ESR ripple.

$$\Delta V_{out_{esr}} = ESR \times \left( \frac{I_{out}}{1 - D_{boost}} + \frac{K_{ind} \times I_{out} \times V_{out}}{2 \times V_{in}} \right) \quad (18)$$

Where:

$\Delta V_{out_{esr}}$  = additional output voltage ripple due to capacitors ESR

ESR = equivalent series resistance of the used output capacitor

$I_{out}$  = maximum output current of the application



---

Dboost = duty cycle calculated with Equation 7

Kind = estimated coefficient that represents the amount of inductor ripple current relative to the

## References

1. *Basic Calculation of a Boost Converter's Power Stage* (SLVA372B)
2. *Basic Calculation of a Buck Converter's Power Stage* (SLVA477)

## Appendix A. Design Example Using TPS63020

### A.1 System Requirements

$V_{out} = 3.3V$   
 $I_{out} = 2A$   
 $V_{inmin} = 2.6V$

$V_{inmax} = 5.5V$   
 Efficiency (3.3V<sub>out</sub> @ 5.5V<sub>in</sub>) = 91%  
 Efficiency (3.3V<sub>out</sub> @ 2.6V<sub>in</sub>) = 74%

### A.2 Duty Cycle

For buck mode duty cycle use equation 1,  $D_{buck} = 0.546$ . For boost mode duty cycle use equation 2,  $D_{boost} = 0.417$ .

### A.3 Inductor Selection

#### Buck

Using Equation 3:

- $L = 0.917\mu H$ , (assuming  $K_{ind} = 0.3$ )

Inductor Selected: 1.0  $\mu H$

#### Boost

Using Equation 4:

- $L = 0.302\mu H$ , (assuming  $K_{ind} = 0.3$ )

### A.4 Maximum Switch Current

#### Buck

Using Equations 5 through 7:

- $D_{buck} = 0.546$
- $I_{ripmax} = 501mA$
- $I_{swmax} = 2.25 A$
- $I_{maxout} = 3.75 A$  which is greater than 2 A

#### Boost

Using Equations 8 through 10:

- $D_{boost} = 0.417$
- $I_{rip} = 452 mA$
- $I_{swmax} = 3.66 A$
- $I_{maxout} = 2.20 A$  which is greater than 2 A

### A.5 Output Voltage Setting

Using equation 11 and assuming  $I_{FB} = 0.01\mu A$ ,  $I_{R1/2}$  minimum is found to be  $1\mu A$ . By assuming  $3\mu A$  for  $I_{R1/2}$ ,  $167k\Omega$  is calculated from equation 12 for R2.  $169k\Omega$  is chosen for R2. Equation 13 then yields  $946k\Omega$  for R1 which,  $953k\Omega$  is chosen for R1. The typical output voltage with these values of resistors is 3.32V.

### A.6 Input Capacitor Selection

Two 10 $\mu F$ , 6.3V, X5R ceramic capacitors are chosen for the design.

## A.7 Output Capacitor Selection

Using equations 14, 16, and 17, the minimum capacitance required is calculated by taking the maximum of these values. Equations 14, 16, and 17 yield 1.04  $\mu\text{F}$ , 1.09  $\mu\text{F}$ , and 11.6  $\mu\text{F}$ . The maximum was the result from equation 17, 11.6  $\mu\text{F}$ . Two 10  $\mu\text{F}$ , 6.3V, X5R, +/- 20% ceramic capacitors, (Murata, GRM188R60J106ME84), were chosen for the output capacitance. This capacitor is commonly chosen in low power DCDC applications by Texas Instruments due to its enhanced DC-bias performance. By using the manufacture's provided information, the combined derated value of the two output capacitors is 12.9  $\mu\text{F}$  which is sufficient for the minimum output capacitance calculated in equation 17. The use a non-enhanced capacitor with the same specs as the one chosen for this design would probably require a third output capacitor.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components which meet ISO/TS16949 requirements, mainly for automotive use. Components which have not been so designated are neither designed nor intended for automotive use; and TI will not be responsible for any failure of such components to meet such requirements.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)