

A Switchable RF Attenuator

A switchable RF attenuator is helpful in making antenna gain comparisons or plotting antenna radiation patterns; attenuation may be switched in or out of the line leading to the receiver to obtain an initial or reference reading on a signal strength meter. Some form of attenuator is also helpful for locating hidden transmitters, where the real trick is pinpointing the signal source from within a few hundred feet. At such a close distance, strong signals may overload the front end of the receiver, making it impossible to obtain any indication of a bearing.

The attenuator of Figs 46 and 47 is designed for low power levels, not exceeding 1/2 watt. If for some reason the attenuator will be connected to a transmitter, a means of bypassing the unit during transmit periods must be devised. An attenuator of this type is commonly called a step attenuator, because any amount of attenuation from 0 dB to the maximum available (81 dB for this particular instrument) may be obtained in steps of 1 dB. As each switch is successively thrown from the OUT to the IN position, the attenuation sections add in cascade to yield the total of the attenuator steps switched in. The maximum attenuation of

any single section is limited to 20 dB because leak-through would probably degrade the accuracy of higher values. The tolerance of resistor values also becomes more significant regarding accuracy at higher attenuation values.

A good quality commercially made attenuator will cost upwards from \$150, but for less than \$25 in parts and a few hours of work, an attenuator may be built at home. It will be suitable for frequencies up to 450 MHz. Double-sided pc board is used for the enclosure. The version of the attenuator shown in Fig 46 has identification lettering etched into the top surface (or front panel) of the unit. This adds a nice touch and is a permanent means of labeling. Of course rub-on transfers or Dymo tape labels could be used as well.

Female BNC single-hole, chassis-mount connectors are used at each end of the enclosure. These connectors provide a means of easily connecting and disconnecting the attenuator.

Construction

After all the box parts are cut to size and the necessary holes made, scribe light lines to locate the inner partitions. Carefully tack-solder all partitions in position. A 25-watt

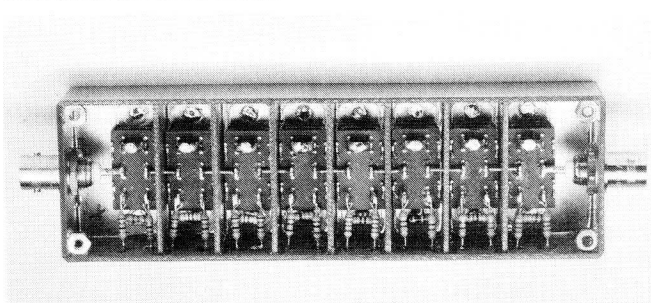
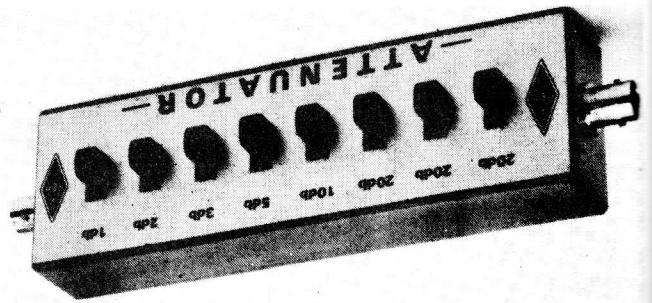


Fig 46—A construction method for a step attenuator. Double-sided circuit-board material, unetched (except for panel identification), is cut to the desired size and soldered in place. Flashing copper may also be used, although it is not as sturdy. Shielding partitions between sections are necessary to reduce signal leakage. Brass nuts soldered at each of the four corners allow machine screws to secure the bottom cover. The practical limit for total attenuation is 80 or 90 dB, as signal leakage around the outside of the attenuator will defeat attempts to obtain much greater amounts. A kit of parts is available from Circuit Board Specialists, PO Box 951, Pueblo, CO 81002.

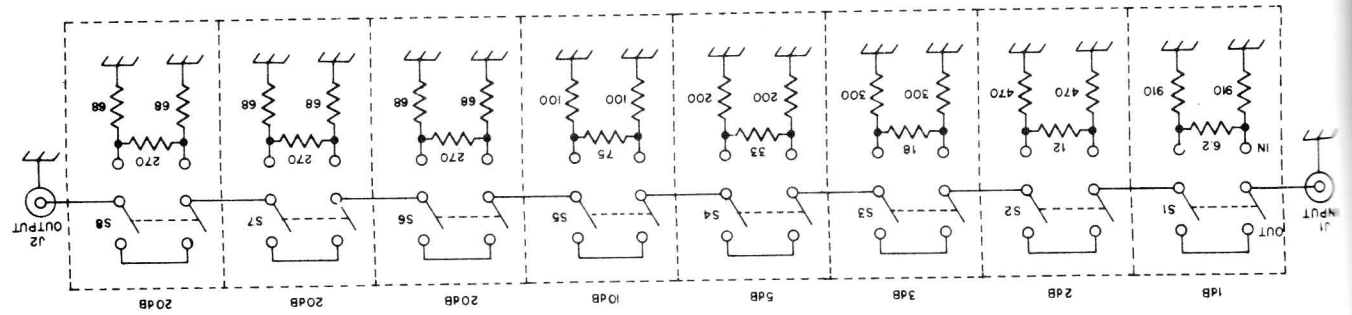


Fig 47—Schematic diagram of the step attenuator, designed for a nominal impedance of 52 ohms. Resistance values are in ohms. Resistors are 1/2-watt, carbon-composition types, 5% tolerance. Broken lines indicate wails of circuit-board material. A small hole is drilled through each partition wall to route bus wire. Keep all leads as short as possible. The attenuator is bilateral; that is, the input and output ends may be reversed.

J1, J2—Female BNC connectors, Radio Shack 278-105 or S1-S8, incl.—DPDT slide switches, standard size. (Avoid submiture or toggle switches.) Stackpole S-5022CD03-0 switches are used here.